

without its complexity. The output impedance is approximately $1\text{ m}\Omega$ at 100 kHz , dropping to a few microhms below 100 Hz . Despite the obvious performance virtues, bootstrapping the reference and op amp is not without some serious application caveats—for example, providing a positive guarantee of circuit startup.

First, you *must* use the op amp in a single-supply mode as shown to prevent possible output state reversal. Second, you should choose level-shift zener diode D_3 for a certain fall-back criterion; namely, the voltage that the output would fall back to should the op amp not initially bias properly. The criterion should provide that, even if IC_1 should momentarily come up in a low-output state, the net bias of the Q_3 - D_3 string will still be greater than V_{REF} . Then, with IC_1 not yet fully active, the bias voltage at Q_3 will force V_{OUT} to start positive. Once V_{REF} is exceeded, IC_1 gains control, and the circuit achieves its desired stable state. A suitable selection criterion for D_3 is to simply make its breakdown voltage similar to that of D_1 , in this case approximately equal to 6.8V .


As shown, the circuit can supply approximately 250 mA with a nominal output of twice V_{REF} or approximately 14V . If you need remote sensing, you can add the remote-sense isolation resistor R_2 at the load point. Breaking the normal sense line at X enables the remote-sensing option, with C_1 added to decouple the sense loop at high frequencies. A negative-output version reverses the diodes and capacitors,

along with the op-amp supply pins, and substitutes complementary transistors. (DI #1974)

To Vote For This Design, Circle No. 370

Reference

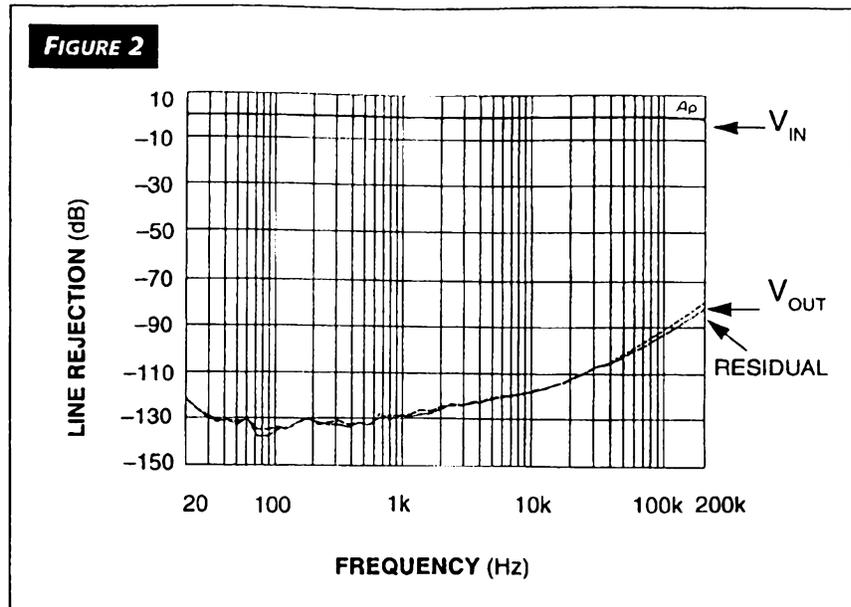1. Jung, Walt, "Regulators for high-performance audio, Parts 1 and 2," *The Audio Amateur*, Issues 1 and 2, 1995.



The output noise of the regulator in Figure 1 is almost indiscernible from the residual noise in the test equipment. Noise output is lower than -130 dB at 100 Hz and approximately -90 dB at 100 kHz .